



例:二阶系统响应的s域求解

$$\frac{\mathrm{d}^2 y(t)}{\mathrm{d}t^2} + 5\frac{\mathrm{d}y(t)}{\mathrm{d}t} + 6y(t) = 2\frac{\mathrm{d}x(t)}{\mathrm{d}t} + 8x(t)$$

已知
$$x(t) = e^{-t}u(t)$$
, $y(0^-) = 3$, $y'(0^-) = 2$, 求 $y(t)$ 。

求解步骤:

- ⇒ 由拉氏变换将时域微分方程变换为s域代数方程
- 求解s域代数方程,求出 $Y_{zi}(s), Y_{zs}(s)$
- ☆ 拉氏反变换, 求出响应的时域表示式



$$y''(t) \qquad 5y'(t) \qquad 6y(t)$$

$$[s^{2}Y(s) - sy(0^{-}) - y'(0^{-})] \qquad +5[sY(s) - y(0^{-})] \qquad +6Y(s)$$

$$= 2sX(s) + 8X(s) \qquad 2x'(t) + 8x(t)$$

$$Y(s) = \frac{sy(0^{-}) + y'(0^{-}) + 5y(0^{-})}{s^{2} + 5s + 6} + \frac{2s + 8}{s^{2} + 5s + 6}X(s)$$



$$Y_{zi}(s) = \frac{3s+17}{s^2+5s+6} = \frac{11}{s+2} - \frac{8}{s+3}$$

$$y_{zi}(t) = \mathcal{L}^{-1}{Y_{zi}(s)} = 11e^{-2t} - 8e^{-3t}, \ t \ge 0$$



$$Y_{zs}(s) = \frac{2s+8}{s^2+5s+6} \cdot \frac{1}{s+1} = \frac{2s+8}{(s+2)(s+3)} \cdot \frac{1}{s+1}$$
$$= \frac{3}{s+1} - \frac{4}{s+2} + \frac{1}{s+3}$$
$$y_{zs}(t) = \mathcal{L}^{-1} \{ Y_{zs}(s) \} = (3e^{-t} - 4e^{-2t} + e^{-3t}) \cdot u(t)$$

$$y(t) = y_{zi}(t) + y_{zs}(t) = 3e^{-t} + 7e^{-2t} - 7e^{-3t}, t \ge 0$$



[练习1]
$$\frac{d^2y(t)}{dt^2} + 7\frac{dy(t)}{dt} + 12y(t) = x(t)$$

已知
$$x(t) = u(t)$$
, $y(0^{-}) = 1$, $y'(0^{-}) = 2$, 求 $y(t)$ 。

[答案]
$$y_{zi}(t) = 6e^{-3t} - 5e^{-4t}, t \ge 0$$
$$y_{zs}(t) = \left(\frac{1}{12} - \frac{1}{3}e^{-3t} + \frac{1}{4}e^{-4t}\right)u(t)$$
$$y(t) = \frac{1}{12} + \frac{17}{3}e^{-3t} - \frac{19}{4}e^{-4t}, t \ge 0$$



[练习2]
$$\frac{d^2y(t)}{dt^2} + 4\frac{dy(t)}{dt} + 4y(t) = 3\frac{dx(t)}{dt} + 2x(t)$$

已知 $x(t) = 4u(t), y(0^-) = -2, y'(0^-) = 3, 求y(t)$ 。

[答案]
$$y_{zi}(t) = -2e^{-2t} - te^{-2t}, \quad t \ge 0$$

 $y_{zs}(t) = (2 + 8te^{-2t} - 2e^{-2t})u(t)$
 $v(t) = 2 - 4e^{-2t} + 7te^{-2t}, \quad t \ge 0$



[练习3]
$$\frac{d^2y(t)}{dt^2} + 4\frac{dy(t)}{dt} + 8y(t) = 3\frac{dx(t)}{dt} + x(t)$$

已知 $x(t) = e^{-t}u(t), y(0^-) = 5, y'(0^-) = 3, 求y(t)。$


[答案]
$$y_{zi}(t) = 5e^{-2t}\cos(2t) + \frac{13}{2}e^{-2t}\sin(2t), \quad t \ge 0$$

$$y_{zs}(t) = \left[-0.4e^{-t} + 0.4e^{-2t}\cos(2t) + 1.7e^{-2t}\sin(2t)\right]u(t)$$

$$y(t) = -0.4e^{-t} + 5.4e^{-2t}\cos(2t) + 8.2e^{-2t}\sin(2t), \quad t \ge 0$$




R、L、C复频域模型

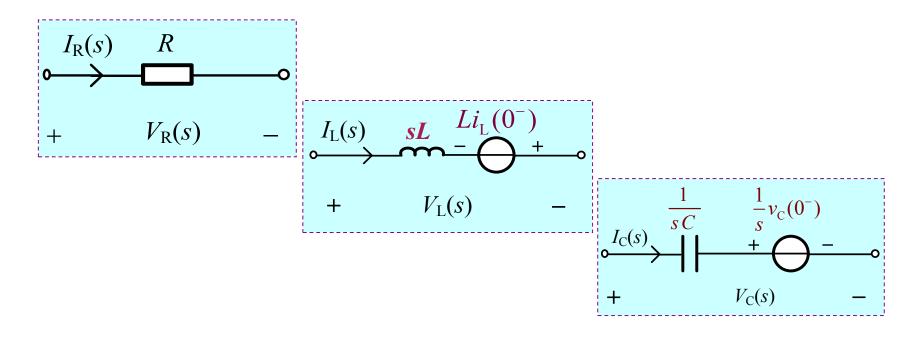



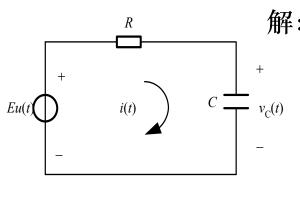图示电路初始状态为 $v_{\rm C}(0^-) = -E$, 求电容两端电压 $v_{\rm C}(t)$ 。



解:建立电路的复频域模型

 $c \stackrel{+}{=} v_{c(t)}$ 由复频域模型写回路方程 $(R + \frac{1}{sC})I(s) = \frac{E}{s} + \frac{E}{s}$

求出回路电流
$$I(s) = \frac{2E}{s(R + \frac{1}{sC})}$$

$$\begin{array}{c|c}
 & & & \\
 & & & \\
\hline
 & & & \\
 & & & \\
\hline
 & & & \\
 & & & \\
 & & & \\
 & & & \\
 & & &$$

电容电压为
$$V_{C}(s) = \frac{I(s)}{sC} - \frac{E}{s} = E(\frac{1}{s} - \frac{2}{s+1})$$

$$v_{C}(t) = E(1 - 2e^{-\frac{1}{RC}t}), t \ge 0$$

$$v_{C}(t) = E(1 - 2e^{-\frac{1}{RC}t}), t \ge$$



$$y''(t) + 7y'(t) + 10y(t) = 2x'(t) + 3x(t)$$

已知 $x(t) = e^{-t}u(t)$, $y(0^-) = 1$, $y'(0^-) = 1$, 由复频域求解:

- (1)零输入响应 $y_{zi}(t)$,零状态响应 $y_{zs}(t)$,完全响应y(t)。
- (2)系统函数H(s),单位冲激响应h(t),并判断系统是否稳定。
- (3)画出系统的直接型模拟框图。



$$y''(t) + 7y'(t) + 10y(t) = 2x'(t) + 3x(t)$$

已知 $x(t) = e^{-t}u(t)$, $y(0^-) = 1$, $y'(0^-) = 1$, 由复频域求解:

(1)零输入响应 $y_{zi}(t)$,零状态响应 $y_{zs}(t)$,完全响应y(t)。

解: (1) 对微分方程两边进行单边拉普拉斯变换得

$$s^{2}Y(s) - sy(0^{-}) - y'(0^{-}) + 7sY(s) - 7y(0^{-}) + 10Y(s) = (2s+3)X(s)$$

$$Y(s) = \frac{sy(0^{-}) + y'(0^{-}) + 7y(0^{-})}{s^{2} + 7s + 10} + \frac{2s + 3}{s^{2} + 7s + 10}X(s)$$

零输入响应的复频域表达式为
$$Y_{zi}(s) = \frac{s+8}{s^2+7s+10} = \frac{2}{s+2} + \frac{-1}{s+5}$$

进行单边拉普拉斯反变换可得 $y_{zi}(t) = \mathcal{L}^{-1}\{Y_{zs}(s)\} = 2e^{-2t} - e^{-5t}, t \ge 0$



综合题: 描述某连续时间LTI因果系统的微分方程为 y''(t)+7y'(t)+10y(t)=2x'(t)+3x(t)

已知 $x(t) = e^{-t}u(t)$, $y(0^-) = 1$, $y'(0^-) = 1$, 由复频域求解:

(1) 案输 λ 响应 v(t). 要状态响应 v(t). 完全响应 v(t)

(1)零输入响应
$$y_{zi}(t)$$
,零状态响应 $y_{zs}(t)$,完全响应 $y(t)$ 。
解: $y(s) = \frac{sy(0^-) + y'(0^-) + 7y(0^-)}{t} + \frac{2s+3}{t} y(s)$

解: $Y(s) = \frac{sy(0^-) + y'(0^-) + 7y(0^-)}{s^2 + 7s + 10} + \frac{2s + 3}{s^2 + 7s + 10}X(s)$ 零状态响应的复频域表达式为

$$Y_{zs}(s) = \frac{2s+3}{(s^2+7s+10)(s+1)} = \frac{1/4}{s+1} + \frac{1/3}{s+2} + \frac{-12/7}{s+5}$$

进行拉普拉斯反变换可得

$$y_{zs}(t) = \mathcal{L}^{-1}{Y_{zs}(s)} = (\frac{1}{4}e^{-t} + \frac{1}{3}e^{-2t} - \frac{7}{12}e^{-5t})u(t)$$
完全响应为 $y(t) = y_{zi}(t) + y_{zs}(t) = \frac{1}{4}e^{-t} + \frac{7}{3}e^{-2t} - \frac{19}{12}e^{-5t}, t > 0$



$$y''(t) + 7y'(t) + 10y(t) = 2x'(t) + 3x(t)$$

已知 $x(t) = e^{-t}u(t)$, $y(0^-) = 1$, $y'(0^-) = 1$, 由复频域求解:

(2)系统函数H(s),单位冲激响应h(t),并判断系统是否稳定。

$$Y_{\rm zs}(s) = \frac{2s+3}{(s^2+7s+10)}X(s)$$

(2) 根据系统函数的定义,可得

$$H(s) = \frac{Y_{zs}(s)}{X(s)} = \frac{2s+3}{s^2+7s+10} = \frac{-1/3}{s+2} + \frac{7/3}{s+5}$$

进行拉普拉斯反变换即得

$$h(t) = \mathcal{L}^{-1}[H(s)] = \left(-\frac{1}{3}e^{-2t} + \frac{7}{3}e^{-5t}\right)u(t)$$

对于因果系统,系统函数的极点为-2,-5位于左半8平面,故系统稳定。




$$y''(t) + 7y'(t) + 10y(t) = 2x'(t) + 3x(t)$$

已知 $x(t) = e^{-t}u(t)$, $y(0^-) = 1$, $y'(0^-) = 1$, 由复频域求解:

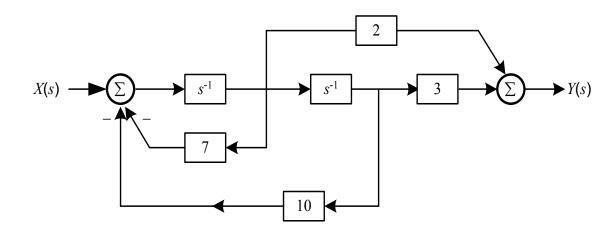(3)画出系统的直接型模拟框图。

解: (3) 将系统函数改写为
$$H(s) = \frac{2s^{-1} + 3s^{-2}}{1 + 7s^{-1} + 10s^{-2}}$$





谢谢

本课程所引用的一些素材为主讲老师多年的教学积累,来源于多种媒体及同事、同行、朋友的交流,难以一一注明出处,特此说明并表示感谢!